

B.Sc. 4th Semester (Honours) Examination, 2022 (CBCS)
Subject: Physics
Paper: CC-X
(Analog Systems and Applications)

Time: 2 Hours

Full Marks: 40

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own word as far as practicable.

Group-A

1. Answer any five questions from the following:

2×5=10

- a) What type of materials are used to construct LED and why?
- b) Mention the importance of Q point of a transistor in CE mode.
- c) Define static and dynamic resistance of a junction diode.
- d) What is Barkhausen's criterion for sustainable oscillation?
- e) Define CMRR and slew rate of an operational amplifier.
- f) Explain how barrier potential will develop in a p-n diode.
- g) Differentiate between open loop and closed loop gain of an amplifier.
- h) Explain the concept of virtual ground.
- i) In what aspects Zener diode differs from a normal p-n junction diode?
- j) Explain different classes of transistor amplifier on the basis of operating point.

Group-B

2. Answer any two questions from the following:

5×2=10

- a) Explain the operation of a bridge full-wave rectifier with proper circuit diagram. What are the merits of this circuit over a normal full-wave rectifier?
- b) "Negative feedback improves the input and output impedance of a transistor amplifier"--- explain.

- c) What are the characteristics of a practical operational amplifier? Design a subtractor using it.
- d) Establish that voltage divider bias is more stable than fixed bias.

Group-C

3. Answer any *two* questions from the following:

10×2=20

- a) i) With proper circuit diagram derive the frequency of oscillation of Hartley oscillator.
ii) A phase shift oscillator is to be operated in the frequency range 40 Hz to 4 kHz. The variable capacitor has a range of 10 pF to 100 pF. Find the required value of resistors. (6+4)
- b) i) Explain the operation of a R-2R ladder D/A converter with proper circuit diagram.
ii) In a differential amplifier with two inputs the output is 2.01 mV when the inputs are 0.11 mV and 0.09 mV but the output is 2 mV when inputs are 0.01 mV and -0.01mV. Find CMRR of the amplifier. (6+4)
- c) i) Draw a neat circuit diagram of a single stage CE amplifier using p-n-p transistor and its h-parameter equivalent circuit.
ii) Obtain the expression of current, voltage and power gain for the above case. (4+6)
- d) i) Explain how we can use zener diode as a voltage regulator for varying load resistance.
ii) State the principle of a photodiode and solar cell. (6+4)