$2 \times 5 = 10$

Full Marks: 40

B.Sc. 4th Semester (Honours) Examination, 2023 (CBCS) Subject : Physics Course : CC-X

Time: 2 Hours

The figures in the margin indicate full marks. Candidates are required to give their answers in their own words as far as practicable.

Group-A

1. Answer *any five* questions from the following:

- (a) What is a hole in semiconductor? How does it move through a crystal?
- (b) What are direct and indirect band gap semiconductors? Give example.
- (c) The mobility of electron is Si at 300 K is $0.130 \text{ m}^2/\text{Vs}$ Calculate the diffusion constant of electron.
- (d) Write down the principle of a photo diode.
- (e) The value of α of a transistor is 0.98. If it changes by 0.5% what would be the corresponding percentage change in the value of β ?
- (f) The power gain of an amplifier is 30 dB. If the input power is 1 mW, what is the output power?
- (g) What do you mean by class A, class B and class C amplifiers?
- (h) What is thermal runway in transistors and how can it be avoided?

Group-B

Answer *any two* questions from the following. $5 \times 2 = 10$

- 2. Explain the concept of diffusion and drift current in a semiconductor. Find the concentration of holes and electrons in a *p*-type germanium if the conductivity is $100 (\Omega m)^{-1}$. [Given: $n_i = 2.5 \times 10^{19}$ electrons/m³, hole mobility $\mu_p = 0.18 \text{ m}^2/\text{Vs}$] $(1\frac{1}{2}+1\frac{1}{2})+2$
- 3. Draw a neat circuit diagram for the collector to base bias arrangement of an n-p-n transistor in CE mode. Obtain an expression for its stability factor. What is the advantage of this circuit? 1+3+1
- 4. Define the four *h*-parameters used in an *h*-parameter equivalent circuit of a transistor. Which of them can be neglected in a simplified model and why? Why *h*-parameter model is not valid at high frequencies?
 3+1+1

Please Turn Over

27723

SH-IV/PHSH/CC-X/23

5. Draw a neat diagram of a two stage RC coupled transistor amplifier. Derive an expression for mid frequency voltage gain. What are the effects of coupling capacitor (C_C) and bypass capacitor (C_E) in the low frequency range? 1+3+1

Group-C

Answer any two questions from the following.

 $10 \times 2 = 20$

6. Draw the circuit diagram of a full wave rectifier with a resistive load, using junction diodes. Calculate the ripple factor. Does it give a perfect dc? What is a filter circuit? Using an ideal zener diode, determine whether the zener diode in the circuit is biased properly. If so, find I_z and I_L.

(1+4)+1+1+3



- 7. With proper diagram, show different current components in a *p-n-p* (or *n-p-n*) transistor under normal biasing condition. Draw the output characteristics of that transistor in CE configuration. Identify and explain different regions in the graph. What is Early effect? 3+2+4+1
- **8.** Explain the concept of virtual ground in an OP-AMP. Is there a virtual ground in non-inverting mode of operation? Explain how an OP-APM can be used as an integrator.

Consider an OP-AMP integrator circuit, with input resistance $R = 100 \text{ k}\Omega$, feedback capacitor $C = 1\mu F$ and power supplies = $\pm 12V$. If input voltage 1 volt is applied at the input inverting terminal determine the nature of output. (2+1)+4+3

9. Describe the working principle of a feedback amplifier with the help of a block diagram. Derive an expression for overall transfer gain.

State Barkhausen Criterion for oscillation.

With a suitable diagram, explain the operation of an R-C phase shift oscillator.

An RC amplifier has mid-frequency gain of 100 and bandwidth of 20kHz. If the amplifier is now provided with a negative feedback network with $|\beta| = 0.02$, what will be the new bandwidth?

(2+2)+1+4+1