

B.Sc. 3rd Semester (Honours) Examination, 2019 (CBCS)**Subject : Physics****Paper : CC-VII****Time: 2 Hours****Full Marks: 40***The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

1. Answer *any five* of the following questions: 2×5=10
- Mention four advantages of integrated circuits.
 - Differentiate between combinational logic circuit and sequential logic circuit.
 - Convert the hexadecimal number 1F1·99A into its equivalent binary and decimal numbers.
 - Verify the Boolean identity $A + \overline{AB} = A + B$.
 - Perform the following subtraction using 2's complement method:

$$48 - 23$$
 - Define a register. Briefly explain how a shift register may be used to introduce a time delay into a system.
 - Consider a memory of size 8 words. Find the binary address of each location.
 - What are the demerits of IC technology?
2. Answer *any two* of the following questions: 5×2=10
- Distinguish between active and passive circuit. Based on the scale of integration classify ICs. How do analog and digital ICs differ? 1+3+1=5
 - Consider two 4-bit numbers A and B with $B > A$. Verify that to subtract A from B it is only required to add B, \overline{A} and 1. Indicate in simple form a 4-bit subtractor obtained from a full adder. 3+2=5
 - What is deflection sensitivity of a CRT? Derive an expression for the deflection sensitivity of a CRT using electro static deflection. 1+4=5
 - Write down the truth table of a three-input EX-OR gate. Hence explain its operation as a parity checker. 3+2=5
3. Answer *any two* of the following questions: 10×2=20
- Explain how to modify a ripple counter so that it divides by N , where N is not a power of 2. Draw the block diagram of a decade ripple counter. Explain its operation. 3+3+4=10

- (b) (i) Minimize the following logic expression and realize using NAND gate

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 7, 8, 9, 10, 11, 12, 13)$$

- (ii) A circuit has three inputs and one output. The output is 1 if any two of the three inputs are 1 and 0 for any other combination of the inputs. Write the output in terms of the inputs A, B, C . Draw a block diagram of this logic circuit. (3+3)+(2+2)=10
- (c) What are the basic building blocks of a 8085 microprocessor? Briefly explain their functions. Briefly describe the addressing modes of a 8085 microprocessor. Write the contents of the registers of 8085 after the completion of the following commands: 'LDA 500H' and then 'MOVB,A'. Initially all the registers have OOH and at address 500H the data stored is 53H. 3+4+3=10
- (d) (i) Explain the operation of decoder and Multiplexer.
(ii) Explain the operation of a BCD to decimal decoder.
(iii) Describe the operation of a priority encoder. 3+4+3=10
-